

2 Amp Driver for 2 DC Motors

D1-D8 should be fast diodes that can handle the stall current of your motor and max reverse voltage equal to your motor voltage

Q1 and Q2 can be any general purpose NPN

2a per motor, 3a peak for less than 100 micro-seconds

